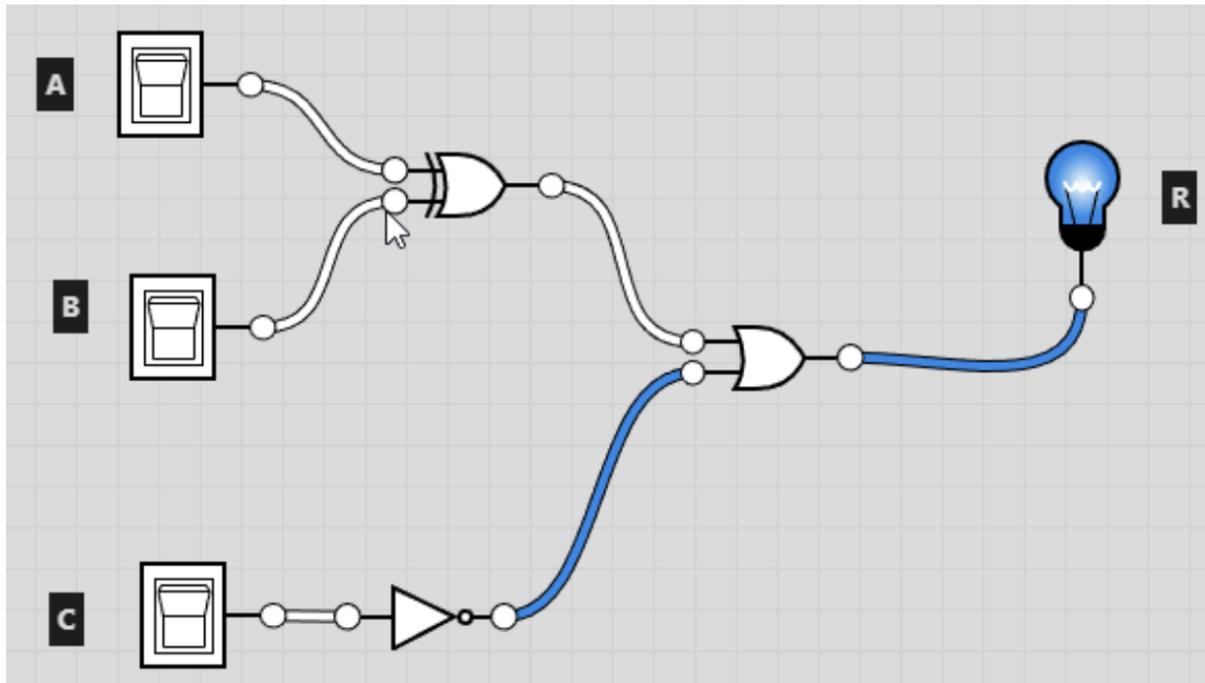


Practice | Logic Gates & Truth Tables


Instructions

Write the corresponding logical expression for the circuit shown.


1)




2)

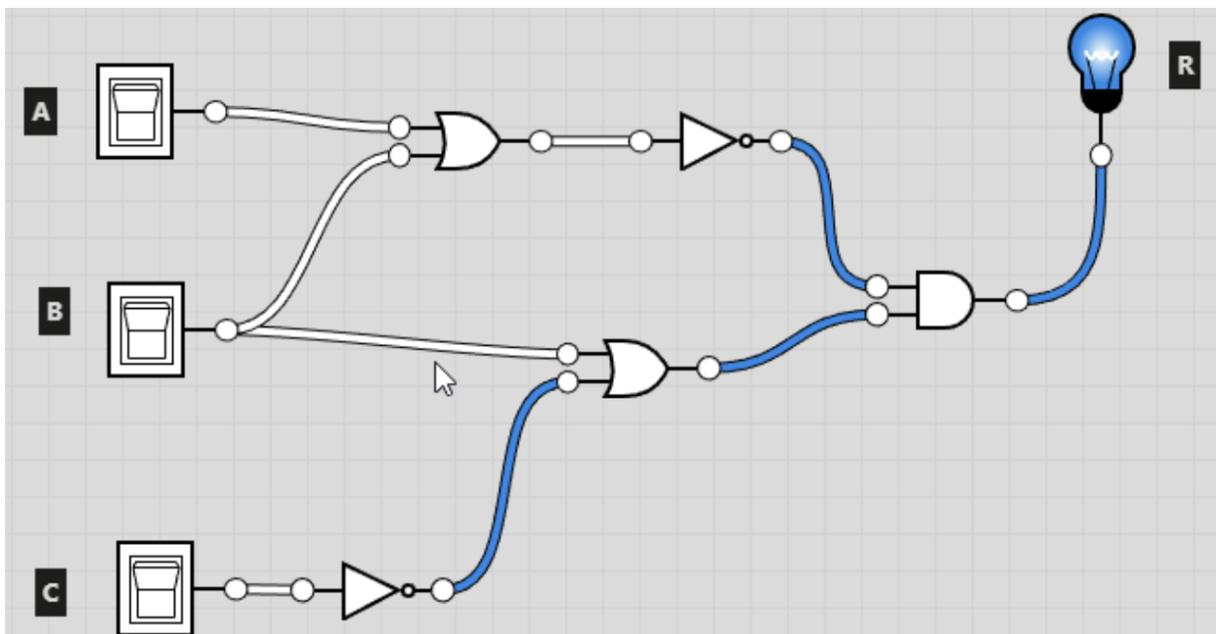


3)

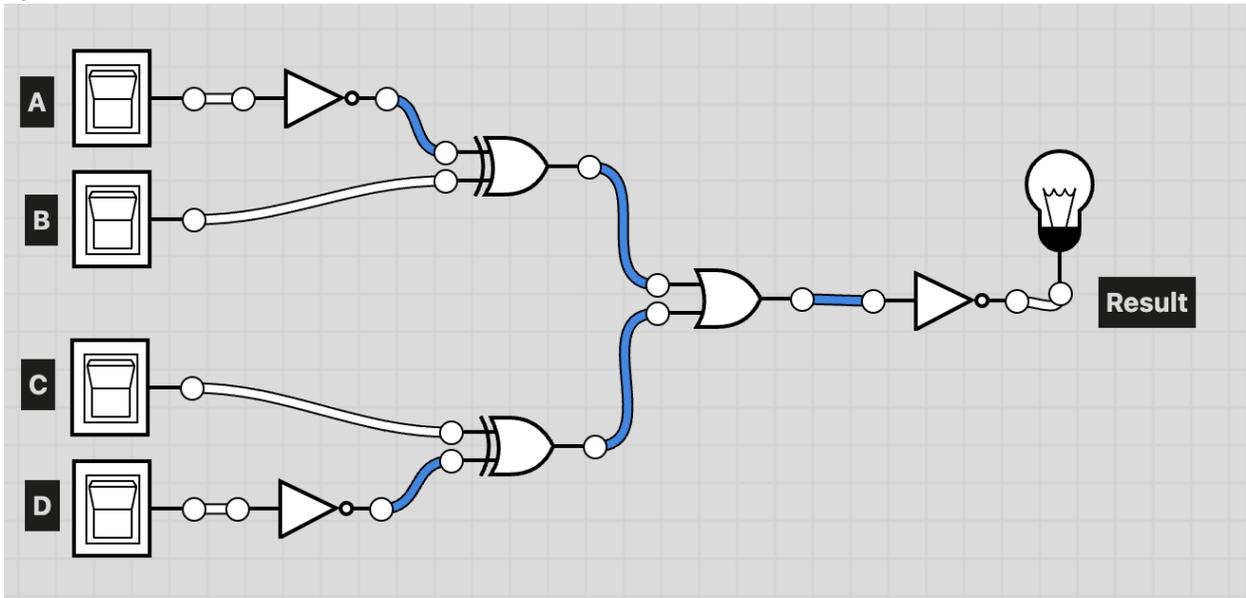

4)

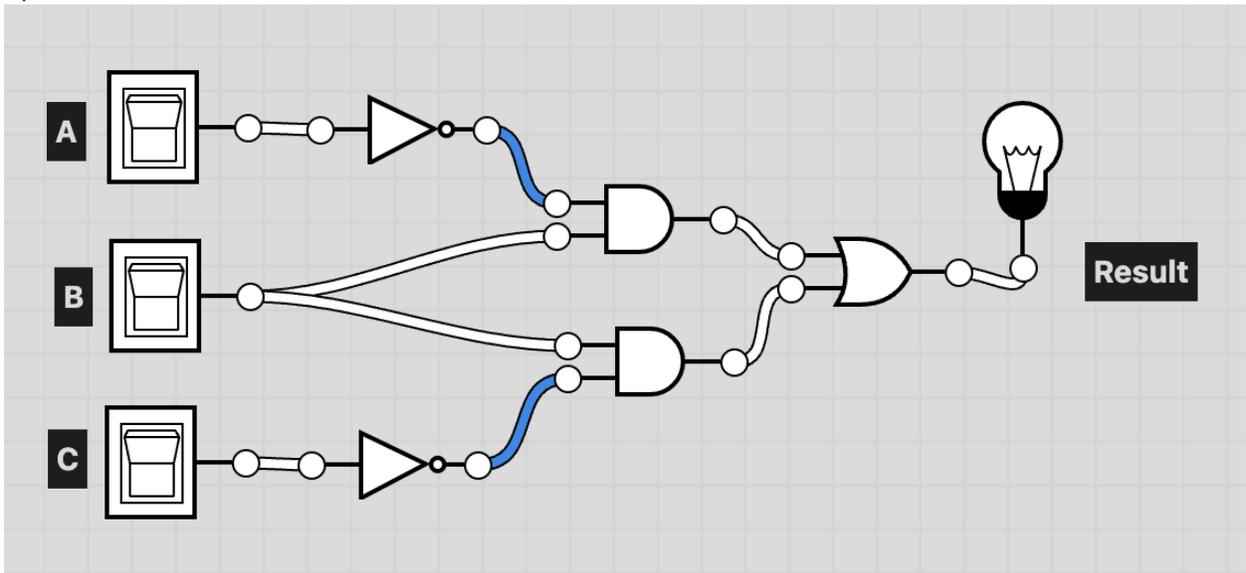

5)

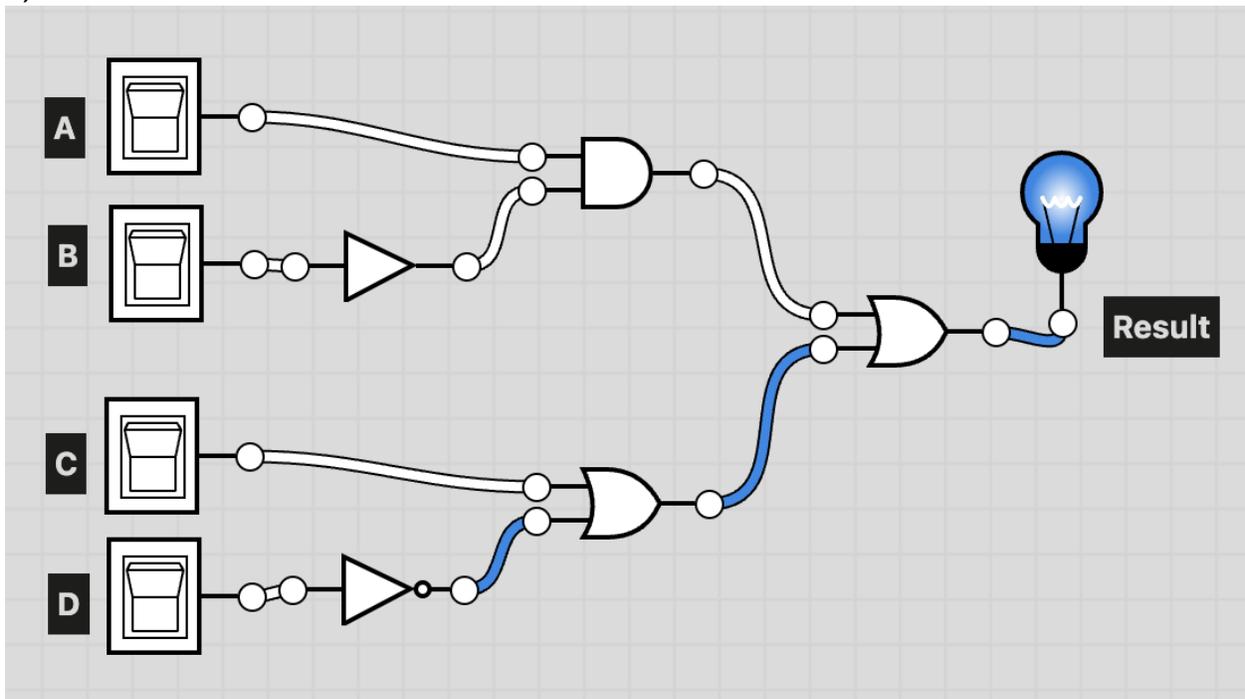

6) $\text{Result} = \sim(A \& B)$

A	B	(A & B)	$\sim(A \& B)$
F	F		
F	T		
T	F		
T	T		

7) $\text{Result} = \sim(A | B)$

A	B	(A B)	$\sim(A B)$
F	F		
F	T		
T	F		
T	T		

8) Result = $(A \& B) \mid (C \& D)$

A	B	C	D	(A & B)	(C & D)	$((A \& B) \mid (C \& D))$
0	0	0	0			
0	0	0	1			
0	0	1	0			
0	0	1	1			
0	1	0	0			
0	1	0	1			
0	1	1	0			
0	1	1	1			
1	0	0	0			
1	0	0	1			
1	0	1	0			
1	0	1	1			
1	1	0	0			
1	1	0	1			
1	1	1	0			
1	1	1	1			

9) Result = $(A \& B) \mid \sim(A \& B)$

A	B	(A & B)	$\sim(A \& B)$	$((A \& B) \mid \sim(A \& B))$
0	0			
0	1			
1	0			
1	1			

10) Result = $(\sim A \mid B) \& (A \mid \sim B)$

A	B	$(\sim A \mid B)$	$(A \mid \sim B)$	$((\sim A \mid B) \& (A \mid \sim B))$
0	0			
0	1			
1	0			
1	1			